

UNI-T

**Test & Measurement
Products and Solutions Provider**

Fi
Test & Measure
Thermal



Electrical Measurement




FEE_Uploader

current meters (Ammeter)

Rules for using current meters:-

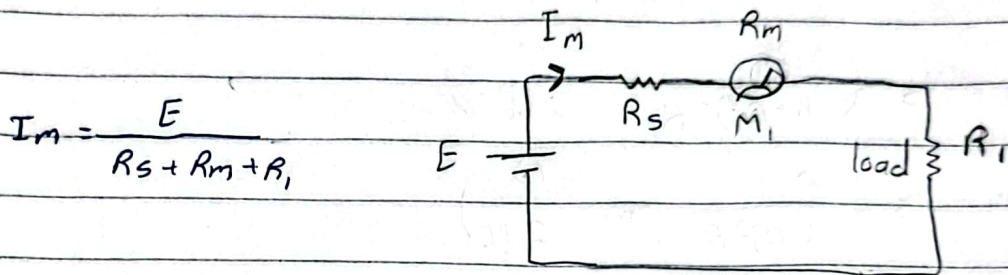
- 1- Connect series with load
- 2- ~~must~~ should full scale current greater than max current
- 3- internal resistance should be smaller than load by 10 times



$$I_m = \frac{E}{R_s + R_m + R_l}$$

ex:- Find the current in M_1
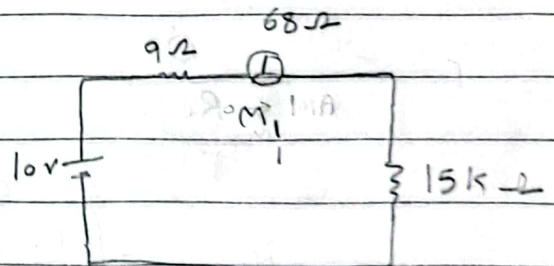
$$I_m = \frac{E}{R_s + R_m + R_l} = \frac{10}{9 + 68 + 15k} = 0.67 \text{ mA}$$





ex:- Find the current

~~For~~ $R_l \gg R_m$

$$R_{total} = R_m + R_s = 68 + 9 = 77 \Omega$$

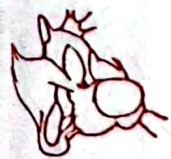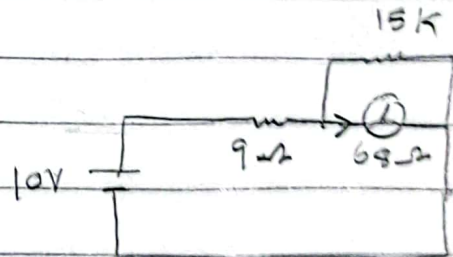
$$I_m = I_{total} = \frac{E}{R_{total}} = \frac{10}{77} = 130 \text{ mA}$$



so to get current meter with high full scale
we should add shunt resistance in parallel with M


$$I_m = I_f \left(\frac{R_s}{R_m + R_s} \right)$$

$$I_f = I_m + I_s$$

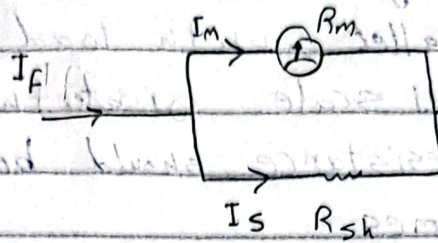

$$R_s = \frac{E_m}{I_s} = \frac{I_m R_m}{I_f - I_m}$$

ex: find I_s and R_s

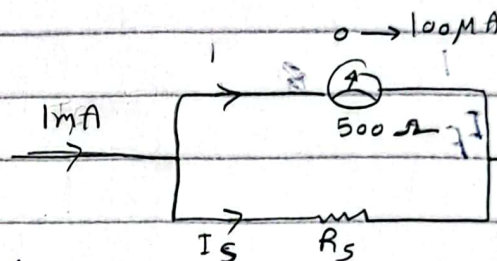


$$I_s = I_f - I_m = 1\text{mA} - 0.1\text{mA} = 0.9\text{mA}$$

$$R_s = \frac{E_m}{I_s} = \frac{I_m R_m}{I_s} = \frac{500 \times 100\mu}{0.9\text{mA}} = 55.6\Omega$$

multiple range ammeter

Full-scale
A → 1mA
B → 10mA
C → 100mA

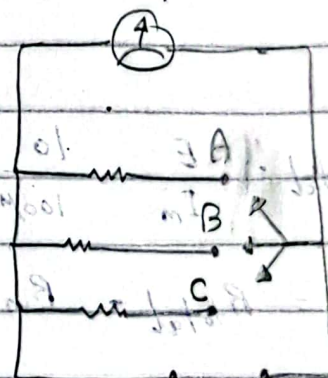

Rules for using volt meter

- 1- Connect parallel with load
- 2- should full scale greater than max Voltage
- 3- internal resistance should be greater than load by 100 times


voltmeter sensitivity (ϕ)

$$\phi = \frac{1}{I_f}$$


$$I_m = \frac{E}{R_m + R_{mx}}$$

$$R_m = \phi \times E$$
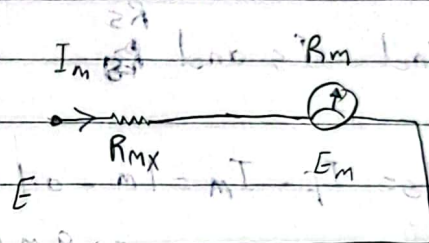
$$E_m = E \left(\frac{R_m}{R_m + R_{mx}} \right)$$




ex - Find R_{mx} and E_m

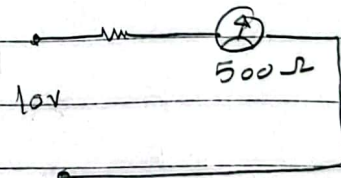



$$R_{total} = \frac{E}{I_m} = \frac{10}{100\mu} = 100,000 \Omega$$

$$R_{mx} = R_{total} - R_m = 100,000 - 500 = 99,500 \Omega$$
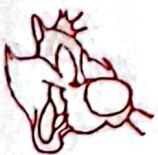
$$E_m = I_m R_m = 100\mu \times 500 = 0.05 V$$



ohmmeter

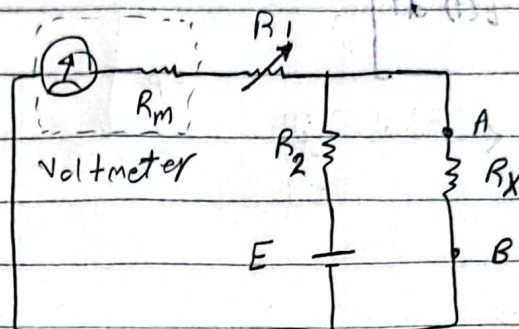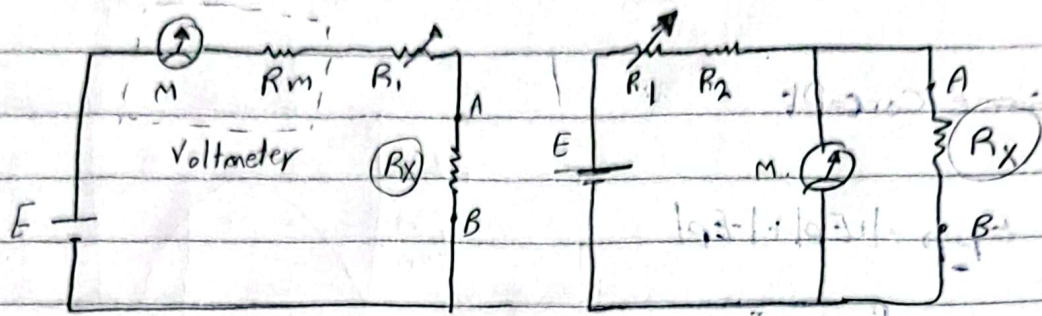

R_x :- resistance that is needed to determine value

multimeter -

instrument is used to measure current, voltage and resistance

ohmmeter + voltmeter + ammeter




AC current

Some Concept

$$E_{pp} = |+E_p| + |-E_p|$$

$$E_{rms} = \sqrt{\frac{1}{T} \int_0^T E(t)^2 dt}$$
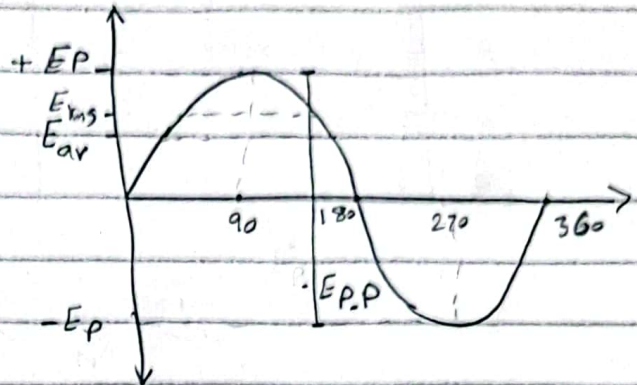
$$= \frac{E_p}{\sqrt{2}} \leftarrow \text{القيل، القيل AC}$$




$$E_{av} = \frac{2E_p}{\pi}$$

$$\text{form Factor (A)} = \frac{E_{rms}}{E_{av}} = \frac{0.7 E_p}{0.6 E_p} = 1.17$$


AC meter

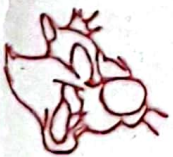- 1- thermocouple AC meter
- 2- Hot wire Ammeter
- 3- electrodynamic meter
- 4- Iron-vane meter



Thermocouple

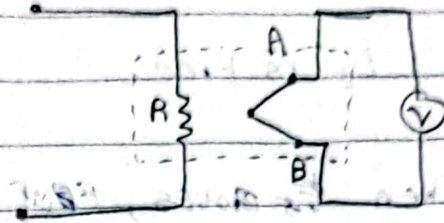depend
~~on~~ on thermocouple
sensor that measure
heat from AC current
then convert to voltage that
useable




measure R.m.s Value

■

Hot-wire

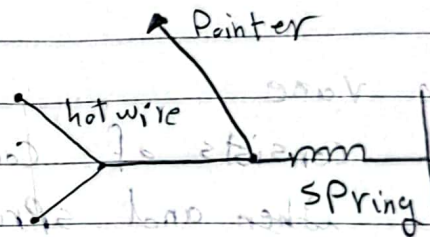when current flow
in hot wire, it expands and
Pointer move to measured value



measure R.m.s value




electrodynamometer

L_3 is free

when ~~it~~ moves, EMF

when current flow L_1, L_2 ,

L_3 moves and current
generate in load

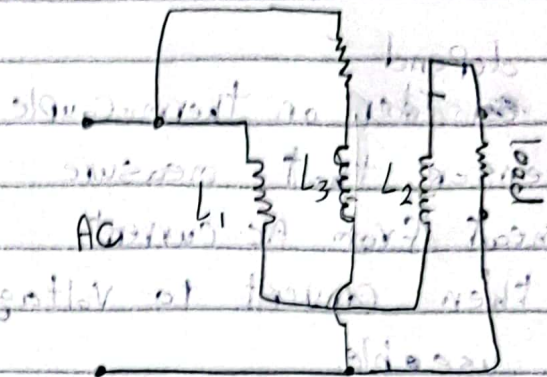

measure I_{av}^2

Iron - vane

consists of coil, movable vane, fixed vane
when and spring

the measured current flows through coil
which produces magnetic field proportional
to the magnitude of current

