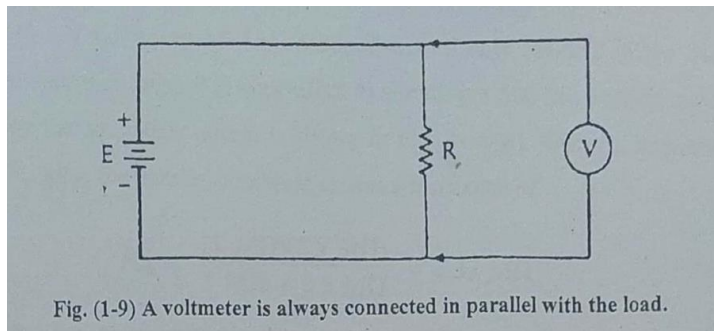


1. An ammeter is connected in **series** with the load.
2. A voltmeter is connected in **parallel** with the load.
3. Name two types of PMMC galvanometer meter movements: **D'Arsonval Movement & Taut Band Movement**
4. The same basic electrical principles govern the behavior of the PMMC meters and **electrodynamometer meters**.
5. The range of an ammeter, milliammeter, or microammeter can be increased if a **shunt resistor** is used in parallel with the meter movement
6. A voltmeter can be made from a DC current meter movement if a **multiplier resistor** is connected in series with the meter movement.
7. Draw the circuit diagram for a simple DC voltmeter:



8. A current meter should have an internal resistance that is **low** compared with external circuit resistances.
9. A voltmeter should have an internal resistance that is **high** compared with external circuit resistances.
10. An ohmmeter may be used in circuits with the power turned off. **(True)**
11. A thermocouple AC ammeter reads the **RMS** value of the AC waveform.
12. Thermocouple ammeters are used at frequencies up to **100 MHz**.
13. A hot-wire ammeter reads the **RMS** value of the AC waveform.
14. A dynamometer is an AC ammeter constructed from a movable coil in the magnetic fields of two stationary coils. All three coils are connected in **series** with each other.
15. The ammeter in Question 14 is calibrated in RMS values but is actually reading **average** values.
16. A **current transformer** is used to extend the current range of the electro-dynamometer type of AC current meter.

17. Iron-vane meters read the **RMS** value of the AC waveform.

18. What happens to the iron-vane meter when DC is measured?

The meter suffers from residual magnetism due to the unidirectional current.

Method to overcome this problem: Use a demagnetizing circuit or alternating current before measuring DC.


19. A rectifier meter reads the **average** value of the alternating current or AC voltage waveform.

20. A diode is often used as the instrumentation rectifier in audio frequency AC meters. **(True)**

21. An AC meter reads different values depending on which way the meter probes are connected. This is called **turnover effect**.

22. A rectifier-type AC voltmeter is operated such that the voltage applied to the rectifier diode is less than 0.7 V (for silicon diodes). This is an example of **square-law** device.

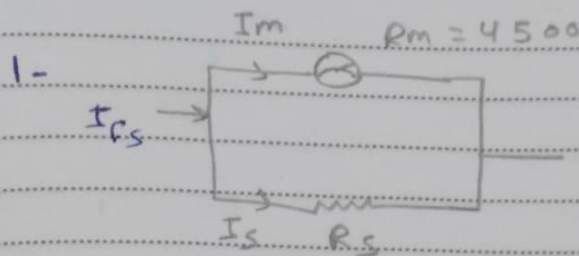23. Which type of AC meter rectifier is immune to both turnover effect and the effects of the phase of harmonics on the reading? **Full-wave square-law rectifier.**



$$I_m = 50 \text{ mA}, \quad R_m = 4500, \quad I_{fs} = 500 \text{ mA}$$

$$\therefore I_s = I_{fs} - I_m = 450 \text{ mA}$$

$$I_s = I_{fs} \frac{R_m}{R_m + R_s}$$


$$450 = 500 \times \frac{4500}{4500 + R_s}$$

$$\therefore R_s + 4500 = 5000$$

$$R_s = 500 \Omega$$

2-
$$I_m = \frac{E}{R_1} = \frac{9}{12} = 0.75 \text{ A}$$

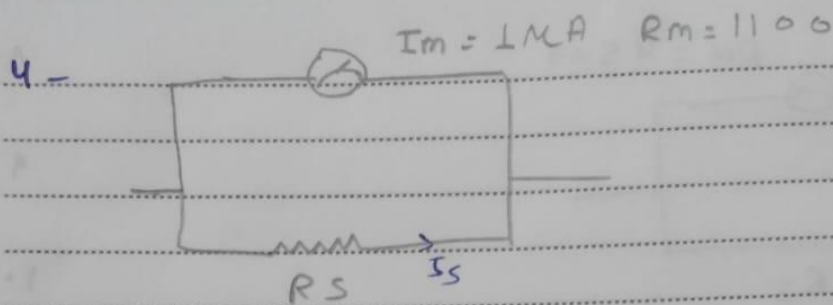3-
$$I_m = \frac{E}{R_{s \text{ source}}} = \frac{12}{22} = 0.54 \text{ A}$$



$$I_{fs} = 100 \mu\text{A}$$

a) ohm's law:-

$$I_s = I_{fs} - I_m$$

$$= 100 - 1 = 99 \mu\text{A}$$

$$E_m = I_m R_m = 10^{-6} \times 1100 = 1.1 \text{ mV}$$

$$\therefore R_s = \frac{E_m}{I_s} = \frac{1.1 \times 10^{-3}}{99 \times 10^{-6}} = 11.1$$

b) current divider:-

$$I_s = I_{fs} \frac{R_m}{R_s + R_m}$$

$$99 = 100 \times \frac{1100}{1100 + R_s}$$

$$1100 + R_s = 1111.11$$

$$\therefore R_s = 11.1 \Omega$$

March

5- نفس فكرة 4

$$6- I_m = \frac{E}{R_m + R_{mX}}$$

$$100 \times 10^{-6} = \frac{100}{1300 + R_{mX}}$$

$$\therefore R_{mX} = 998700 \Omega$$

$$7- 100 \times 10^{-6} = \frac{2}{1300 + R_{mX}}$$

$$R_{mX} = 18700 \Omega$$

$$8- \phi = \frac{1}{I_{FS}} = \frac{1}{30 \times 10^{-6}} = \frac{1}{30} \text{ M } \Omega / \text{V}$$

$$9- R_M = E \phi$$

$$= 50 \times 20,000 = 1 \text{ M } \Omega$$